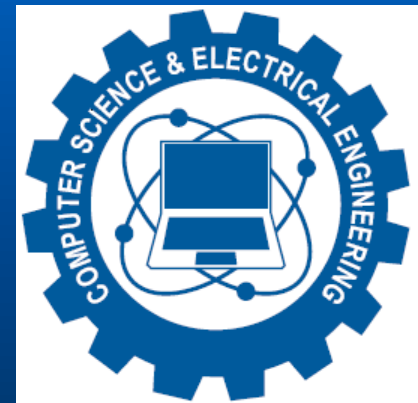



Basic Parallel Circuits/Networks




What is a Parallel Circuit?

- circuit whose current flows along more than one path (branches)
- current is split up through each path (branch)
- voltage is the same across the same path (branch)
- combined resistance is equal to a fraction of the individual resistors

Multiple Path

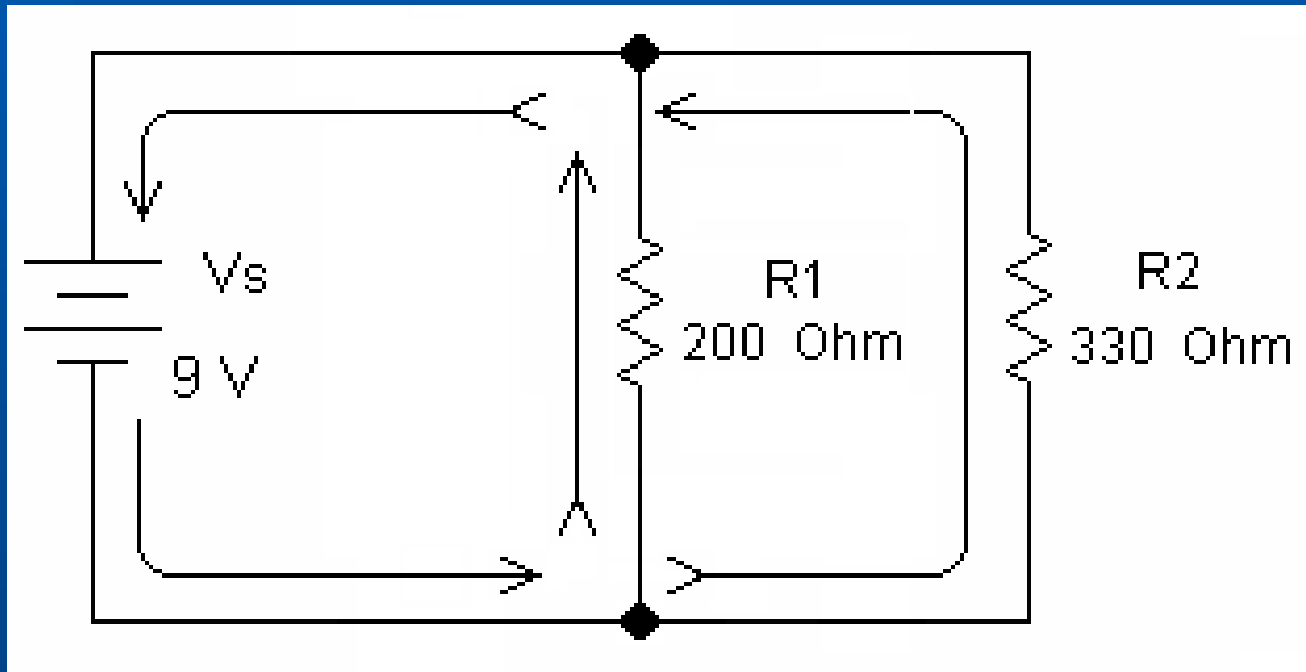

Same Voltage

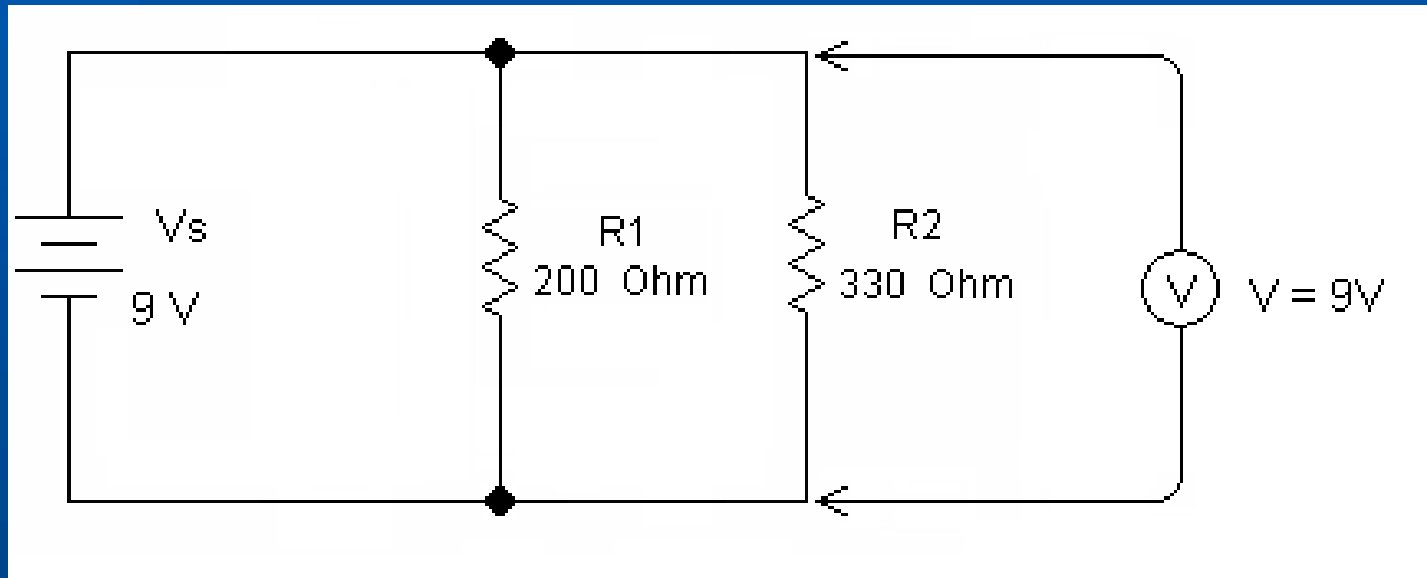


Combined Resistance (R_T)

$$\text{Combined Resistance in Parallel} = 1 / (1/R_1) + (1/R_2)$$

$$R_T = 1 / (.005) + (.003)$$

$$124.5 \Omega = 1 / (.008)$$

Combined Resistance

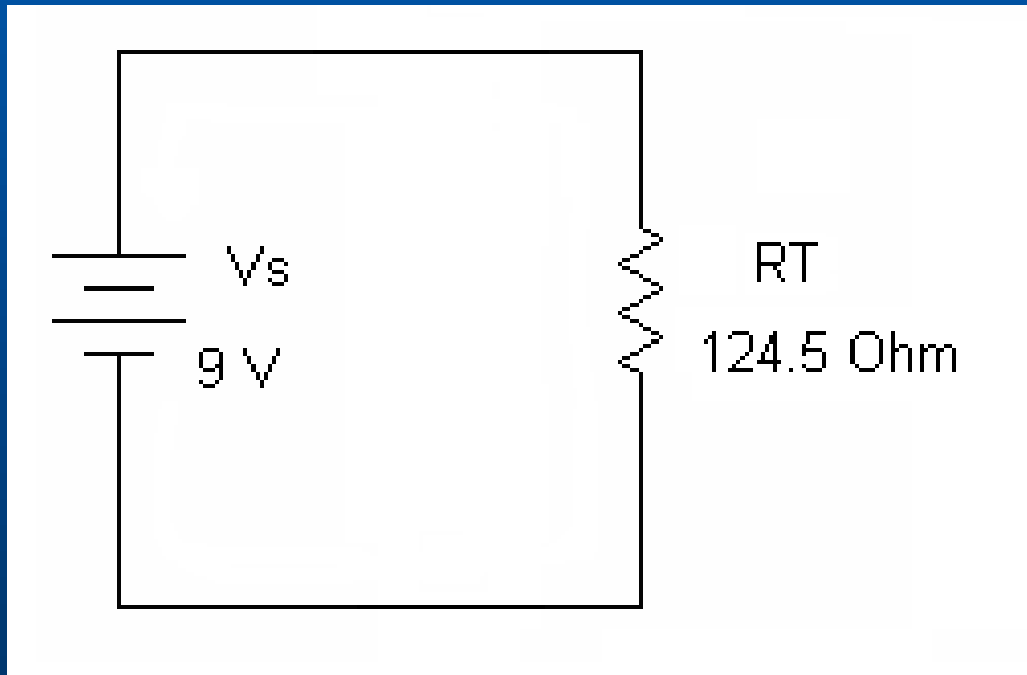


Total Current (I_T)

$$I_T = V_S \div R_T$$

$$.07\mathcal{A} = 9\mathcal{V} \div 124.5\Omega$$

Split Current

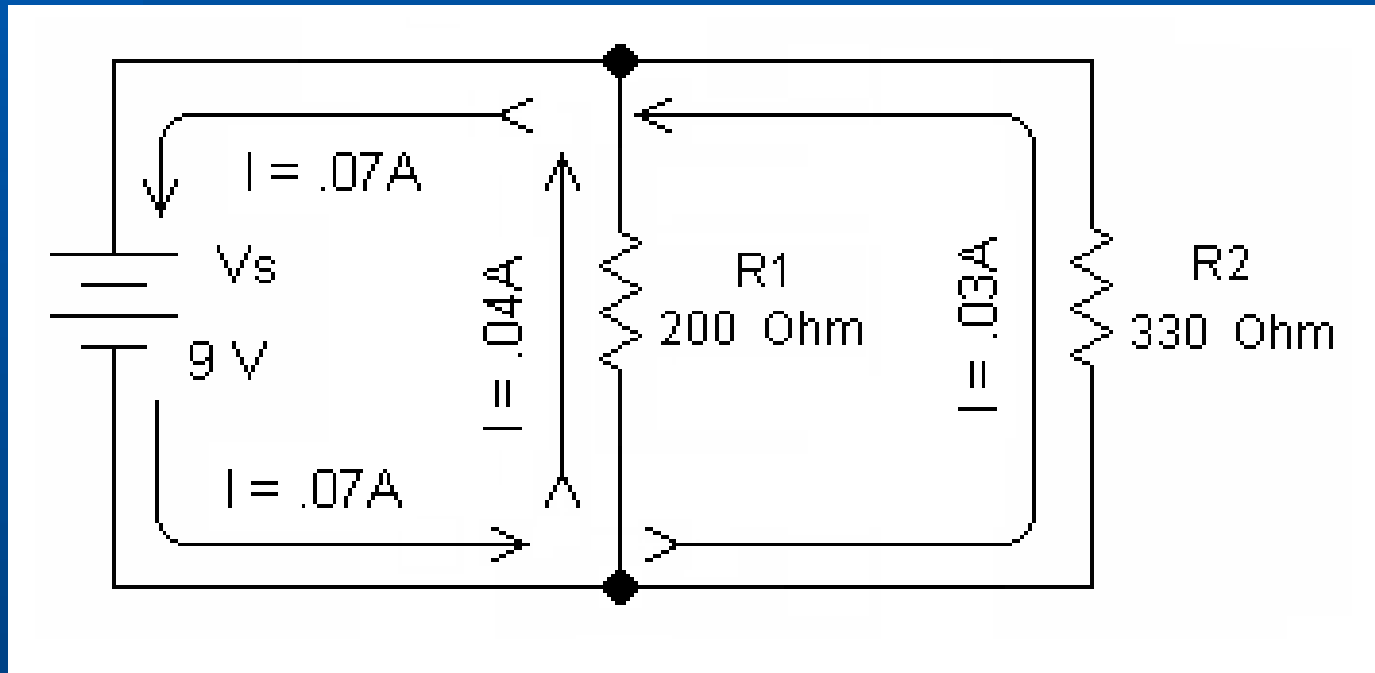

Split Currents (I_{R1} and I_{R2})

$$I_{R1} = V_S \div R_1$$

$$.04\mathcal{A} = 9\mathcal{V} \div 200\Omega$$

$$I_{R2} = V_S \div R_2$$

$$.03\mathcal{A} = 9\mathcal{V} \div 330\Omega$$