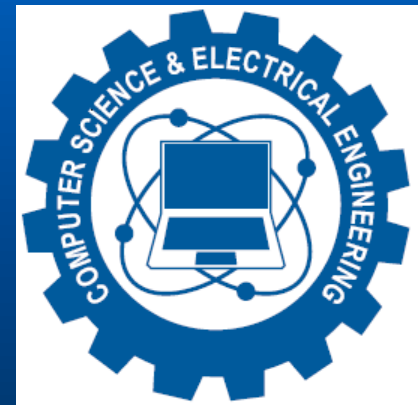



Basic Series Circuits/Networks




What is a Series Circuit/Network?

- **circuit whose current flows along one and only single path**
- **current is the same at any point within the same path and through any resistor**
- **combined resistance is equal to the sum of all the resistors**
- **each resistor has a voltage dropped across it**

Single Path

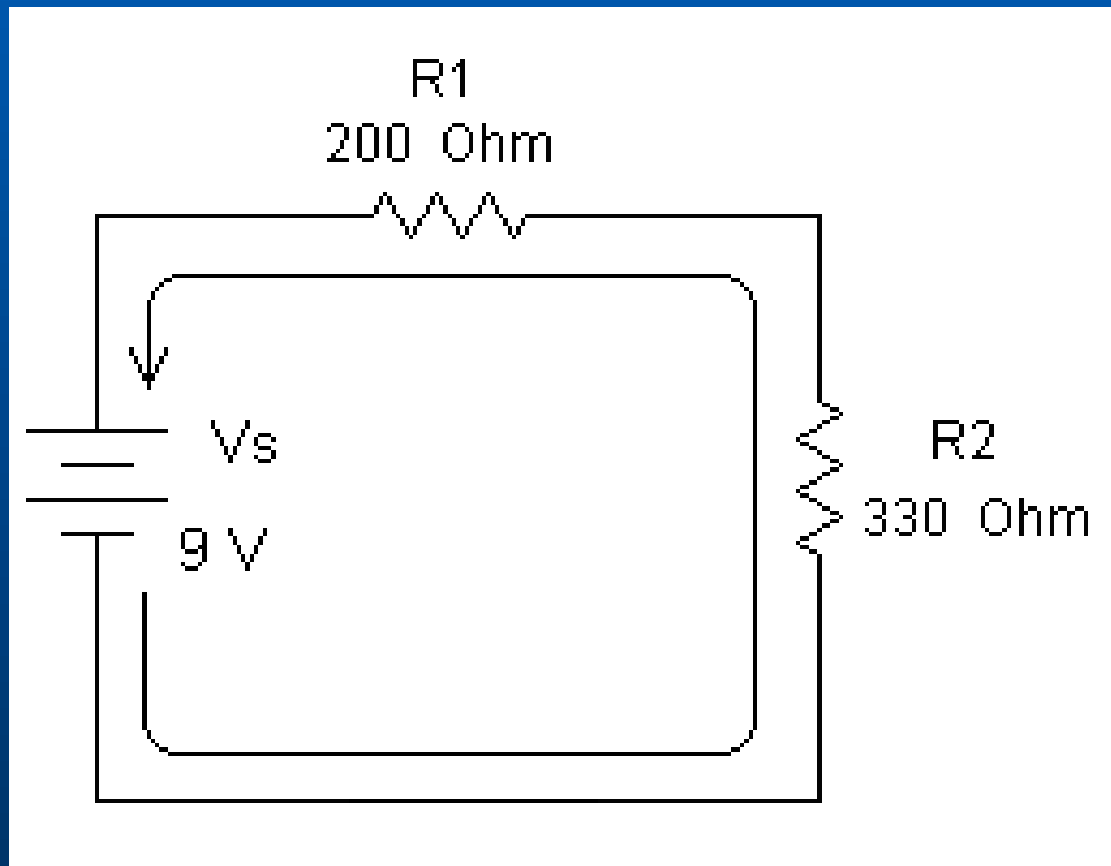

Same Current

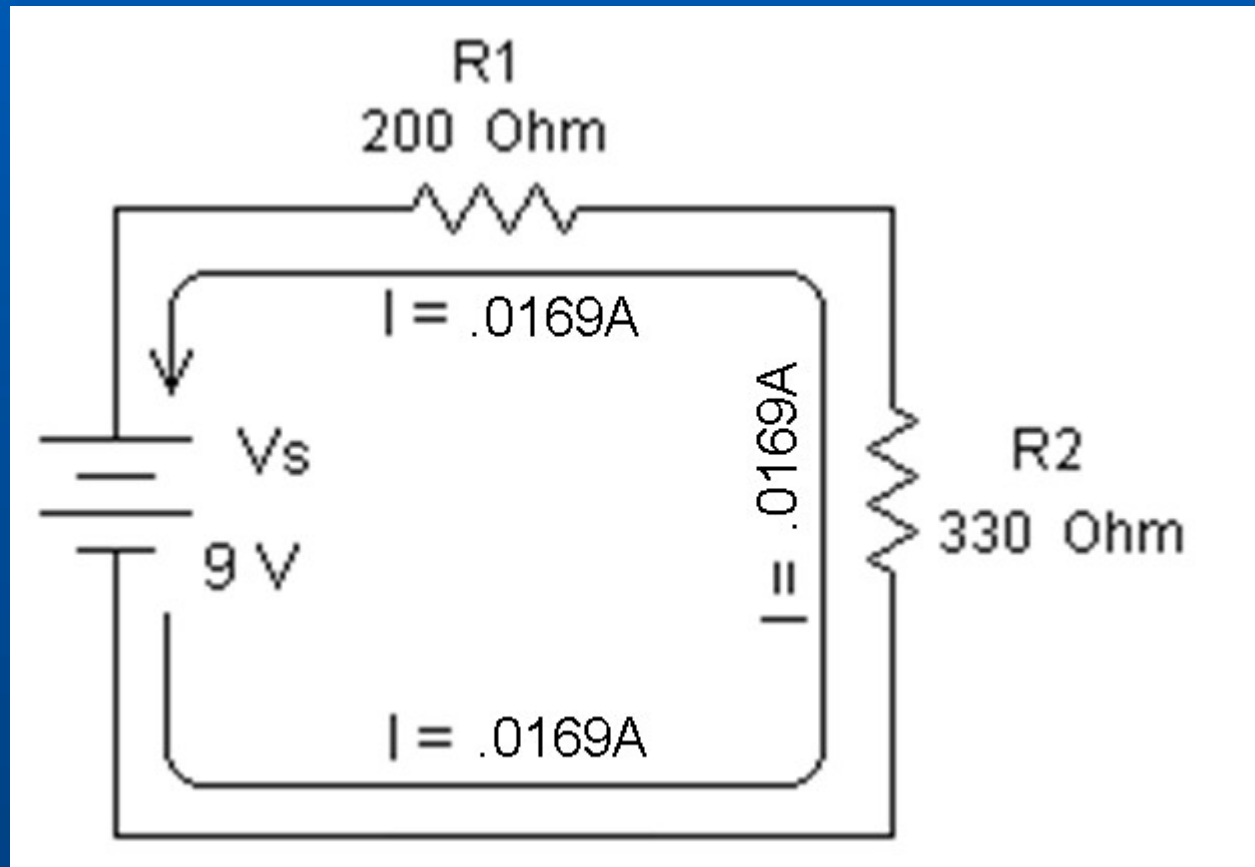


Combined Resistance (R_T)

Combined Resistance in Series = $R_1 + R_2$

$$530\Omega = 200\Omega + 330\Omega$$

Combined Resistance

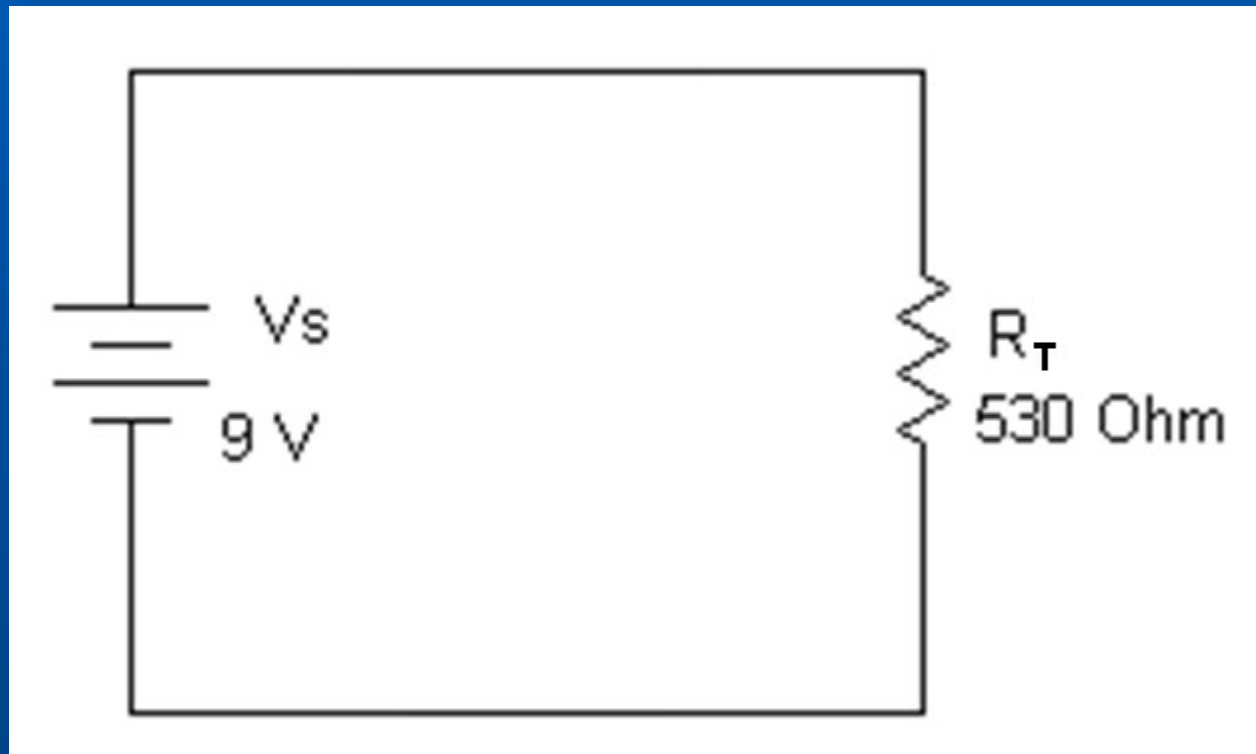


Total Current (I_T)

$$\textit{Total Current} = V_S \div R_T$$

$$.016\mathcal{A} = 9\mathcal{V} \div 530\Omega$$

Same Current

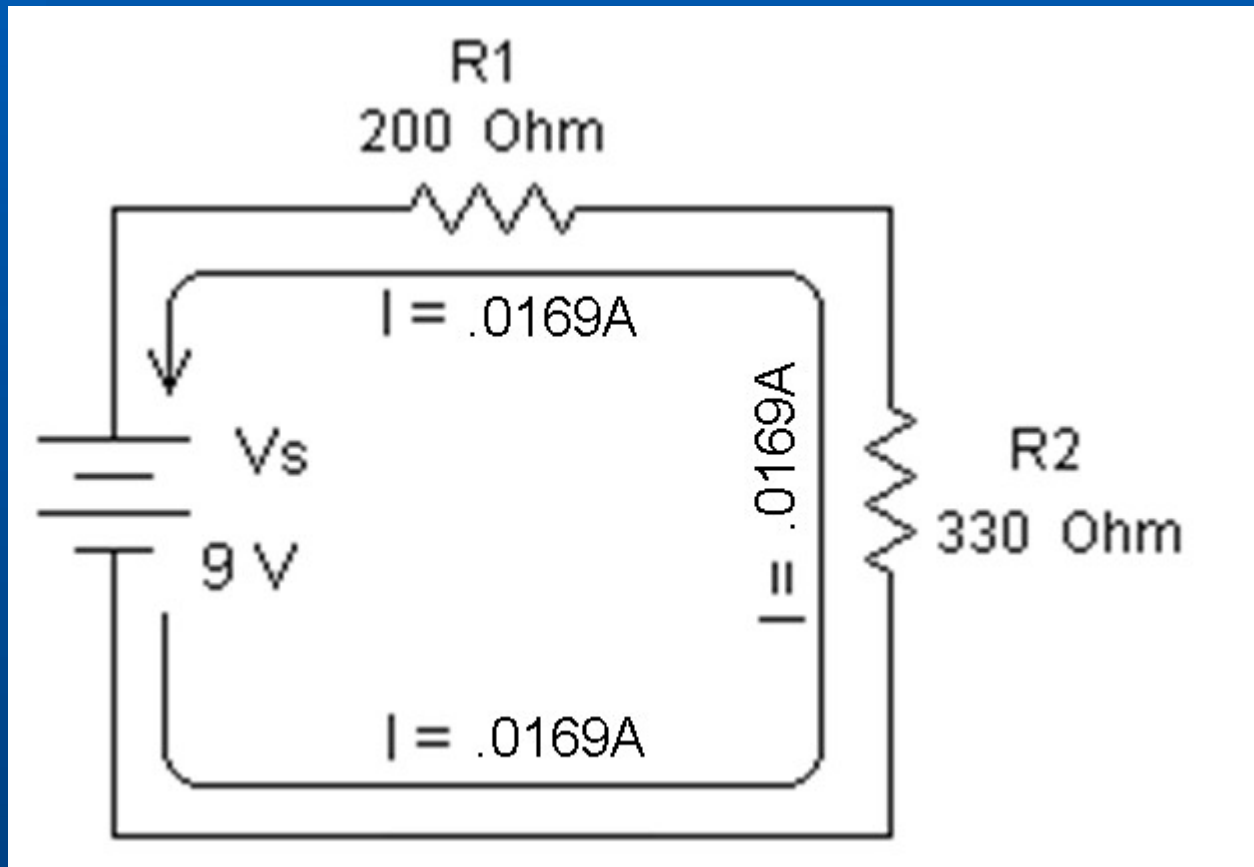

Voltage Drops (V_{R1} and V_{R2})

$$V_{R1} = I_T \times R_1$$

$$3.2\mathcal{V} = .016\mathcal{A} \times 200\Omega$$

$$V_{R2} = I_T \times R_2$$

$$5.28\mathcal{V} = .016\mathcal{A} \times 330\Omega$$